

# Calc Project Overview

Design Specs

# Overview of Calc designs


- Two designs are provided
  - Calc1
  - Calc2

# Calc1

- Calc1 is a simple 4-port calculator.
- Each port can send in 1 command at a time.
- The commands consist of add, subtract, shift left, and shift right.
- The operand data accompanies the commands.
- Since there are 4 ports, there can be up to 4 outstanding commands at once.

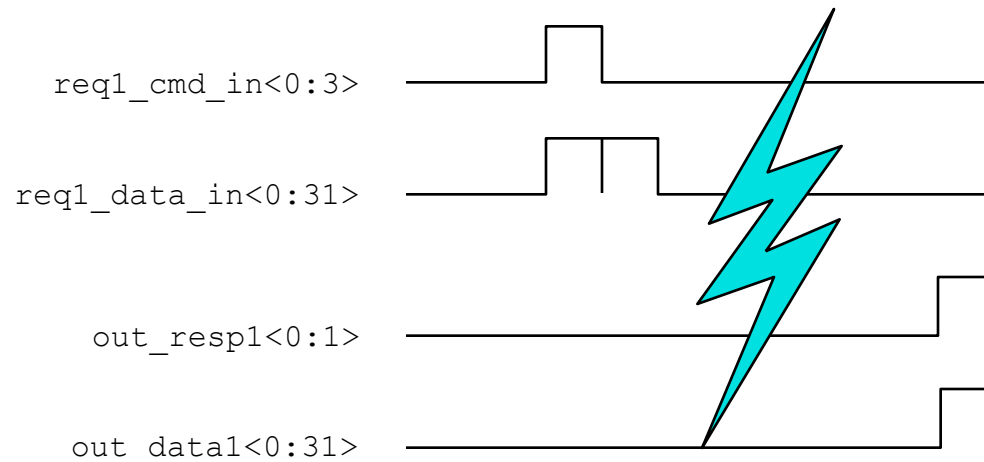
# Calc1

- The input/Output timing on a single port is as follows:



 
# Calc1

- The lightning bolt represents “some number of cycles passing.”



 
# Calc1

- A second request from the same port is prohibited until the response from the first command is received.


 
# Calc1

- Internally, there are two ALUs: one that processes all add commands, and the second for all shift commands. Priority logic dispatches the individual commands to the ALUs.



# Calculator Design

- ☒ Calculator has 4 functions:
  - Add
  - Subtract
  - Shift left
  - Shift right
- ☒ Calculator can handle 4 requests in parallel
  - All 4 requestors use separate input signals
  - All requestors have equal priority
  - Each port must wait for its response prior to sending the next command



# Calculator Design

## ☒ I/O Description

- Input commands:
  - 0 - No-op
  - 1 - Add operand1 and operand2
  - 2 - Subtract operand2 from operand1
  - 5 - Shift left operand1 by operand2 places
  - 6 - Shift right operand1 by operand2 places
- Input Data
  - Operand1 data arrives with command
  - Operand2 data arrives on the following cycle


# Calculator Design

## Outputs

- Response line definition
  - 0 - no response
  - 1 - successful operation completion
  - 2 - invalid command or overflow/underflow error
  - 3 - Internal error
- Data
  - Valid result data on output lines accompanies response (same cycle)

# Calculator Design

## Input/Output timing

 

Each port must wait for its response prior to sending the next command!

# Calculator Design


## Other information

- Clocking
  - When using a cycle simulator, the clock should be held high (c\_clk in the calculator model)
  - The clock should be toggled when using an event simulator
- Calculator priority logic
  - Priority logic works on first come first serve algorithm
  - Priority logic allows for 1 add or subtract at a time and one shift operation at a time

# Calculator Design
 
## ☒ Other information (con't)

- Resets
  - Hold reset(1:7) to '1111111'b at start of testcase for seven cycles.
  - During the reset period, outputs of the calculator should be ignored
- Shift operation
  - Only the low order 5 bits of the second operand are used
- Arithmetic operations are unsigned



# Calc2

- The second design, Calc2, is much like the first, except that each port may now have up to 4 outstanding commands at a time.

# Calc2

- Each command from a port is sent in serially (one at a time), but the calc log may respond “out of order,” depending upon the internal state of the queues.




# Calc2

- As a result, each command is now accompanied by a 2-bit tag, which identifies the command when the response is received.


# Calc2

- A possible timing diagram:

 

 
# Calc2

- The lightning bolt represents “some number of cycles passing.” The data accompanies a successful response signal.



 
# Calc2

- A timing diagram of back-to-back commands might look like:



 
# Calc2

- The lightning bolt represents “some number of cycles passing.”



 
# Calc2

- The data accompanies a successful response signal. Responses may or may not be in order, but the tags will identify which command the response is for.


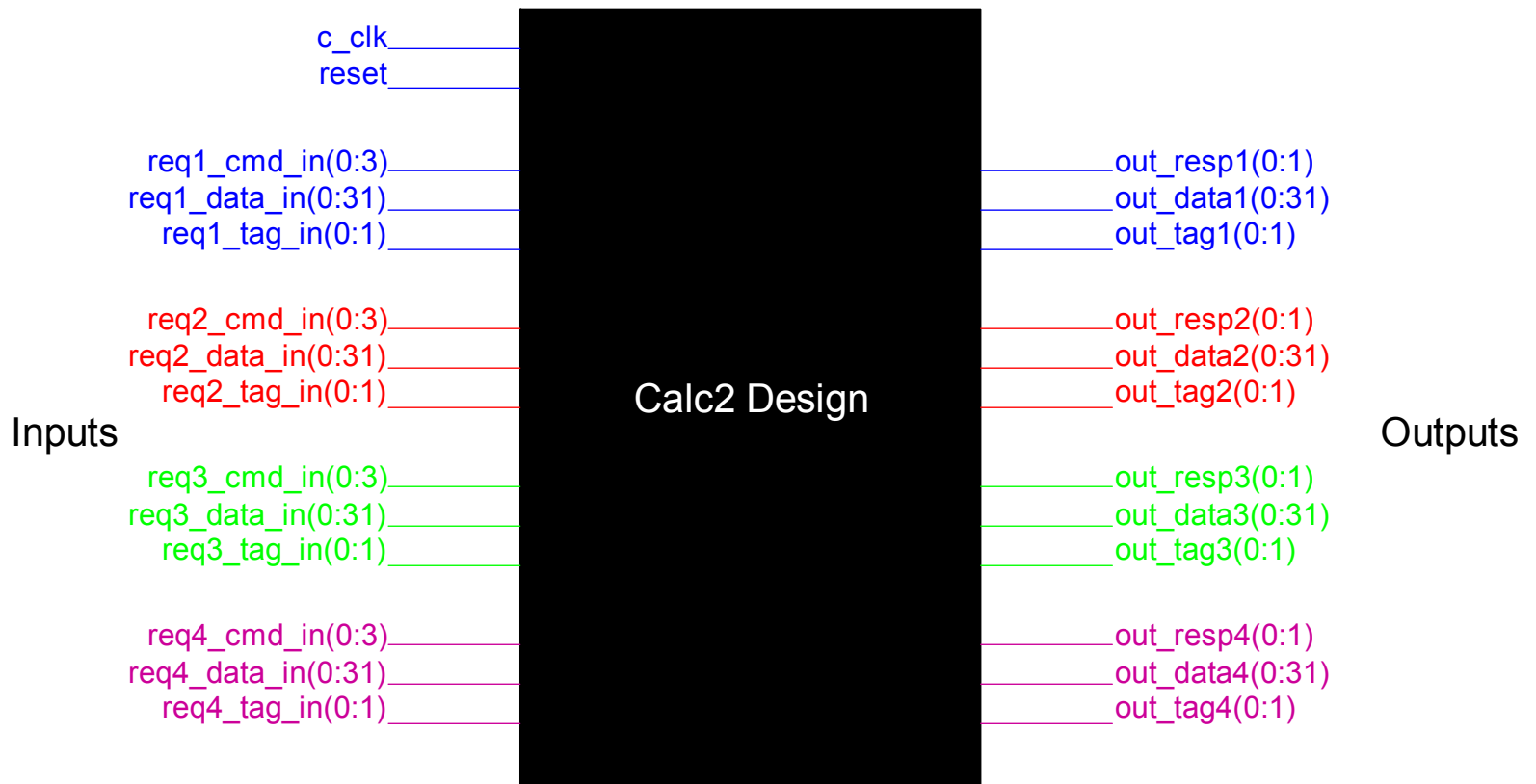
# Calc2

- There may be up to 16 commands outstanding at once (4 ports, 4 commands each).
- As in Calc1, the commands are add, subtract, shift left, and shift right.





# Functional Verification

- Test Plan
- Use SystemVerilog to build your verification environment for Calc1,Calc2.
- Your environment should be class based.
- You should use:
  - Interface
  - Clocking blocks that is sensitive to the falling edge of the clock, and all I/O that are synchronous to the clock
  - A modport for the testbench called master, and modport for the DUT called slave

# Functional Verification

- Random verification
- Functional Coverage
- You need to report all the bugs founds in Calc1,Calc2.

# Functional verification

- Submit:
  - Report for all students
  - All SV code